

# Current divider single IEC source

# Current divider

Current law is not valid since the current divider is complex...


$$I_{iec} \neq I_1 + I_2$$

$$\left. \begin{aligned} I_1 &= I_{iec} \cdot \frac{\underline{Z}_1}{\underline{Z}_1 \parallel \underline{Z}_2} \\ I_2 &= I_{iec} \cdot \frac{\underline{Z}_2}{\underline{Z}_1 \parallel \underline{Z}_2} \end{aligned} \right\} I_{iec} = |\underline{I}_1 + \underline{I}_2|$$

... but the angle information gets discarded afterwards

$$I_1 = |\underline{I}_1| \quad I_2 = |\underline{I}_2|$$


$$I_{iec} = |\underline{I}_1 + \underline{I}_2| \neq |\underline{I}_1| + |\underline{I}_2| = I_1 + I_2$$

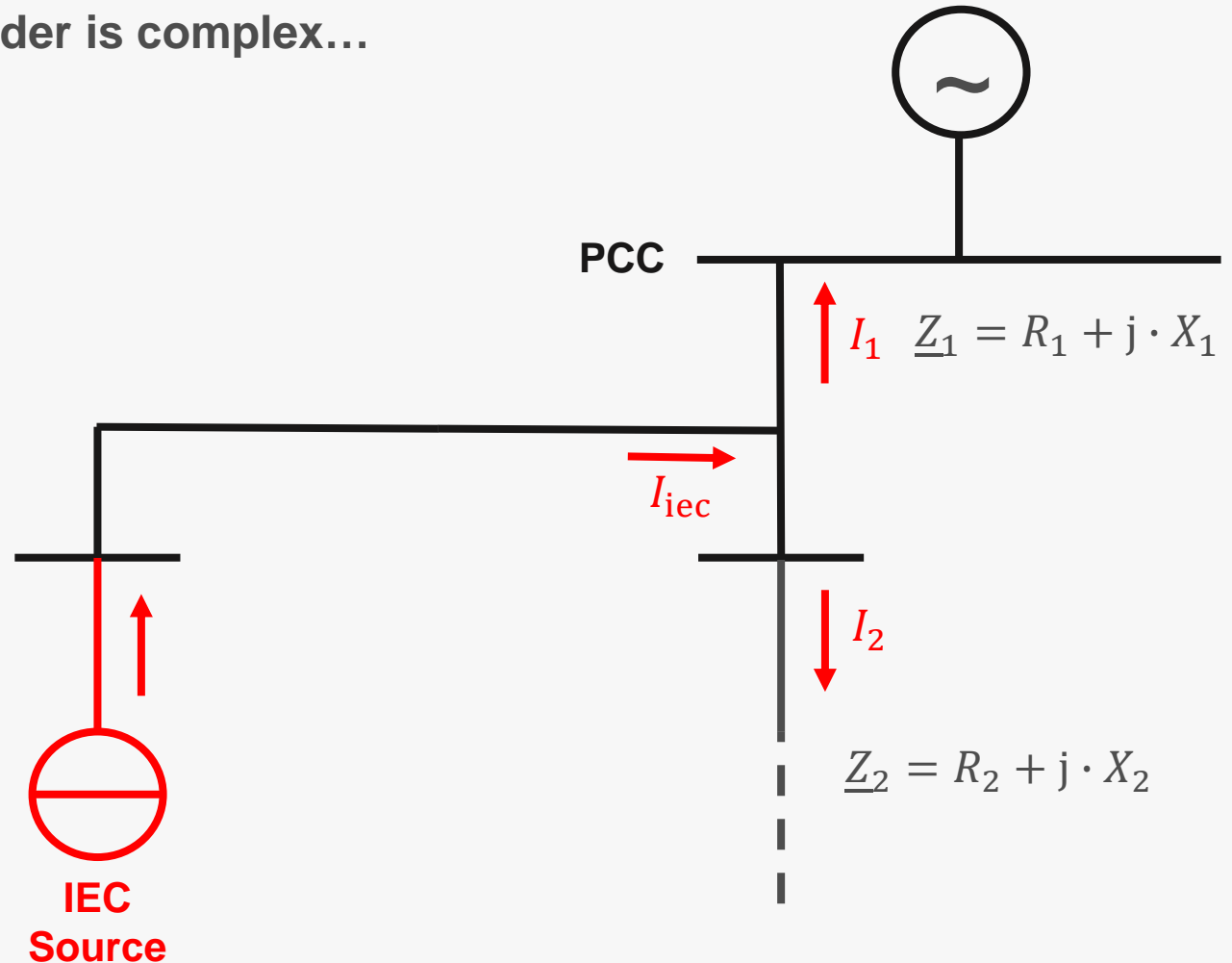

# Summation law with multiple IEC sources

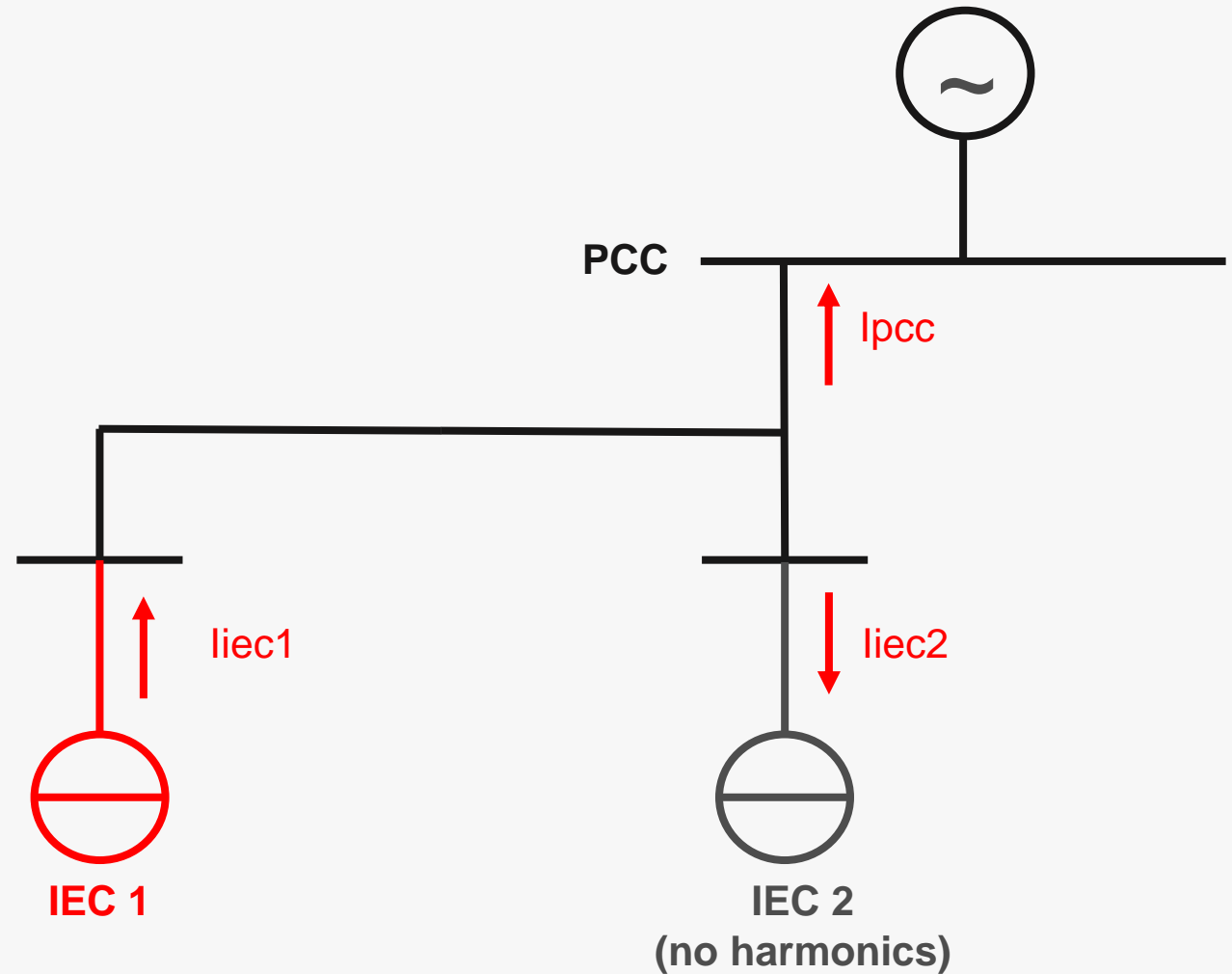
# Summation law with multiple IEC sources

1<sup>st</sup> calculation with only the first IEC source


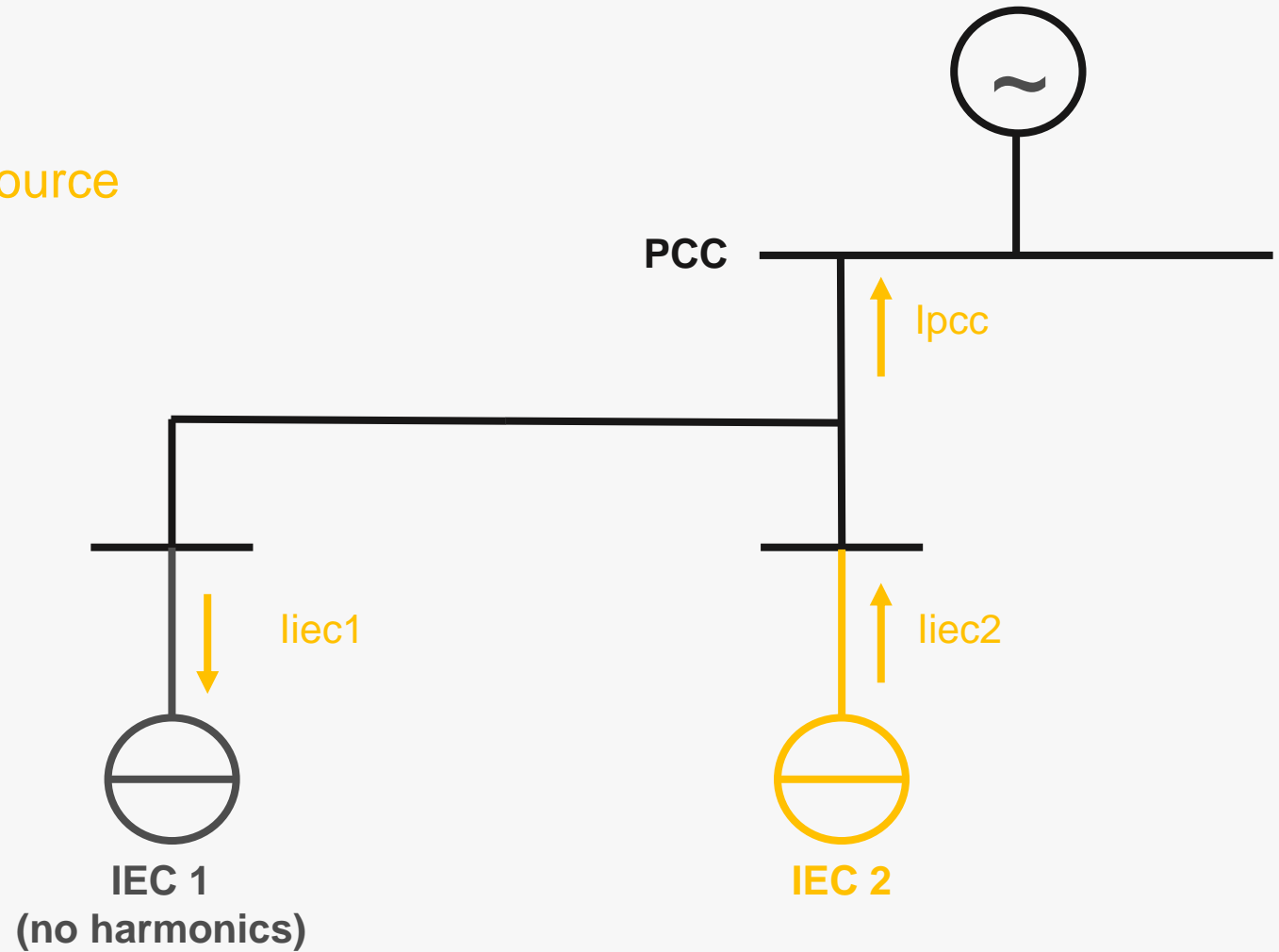
# Summation law with multiple IEC sources

2<sup>nd</sup> calculation with only the second IEC source




# Summation law with multiple IEC sources



1<sup>st</sup> calculation with only the first IEC source

2<sup>nd</sup> calculation with only the second IEC source

Summation Law

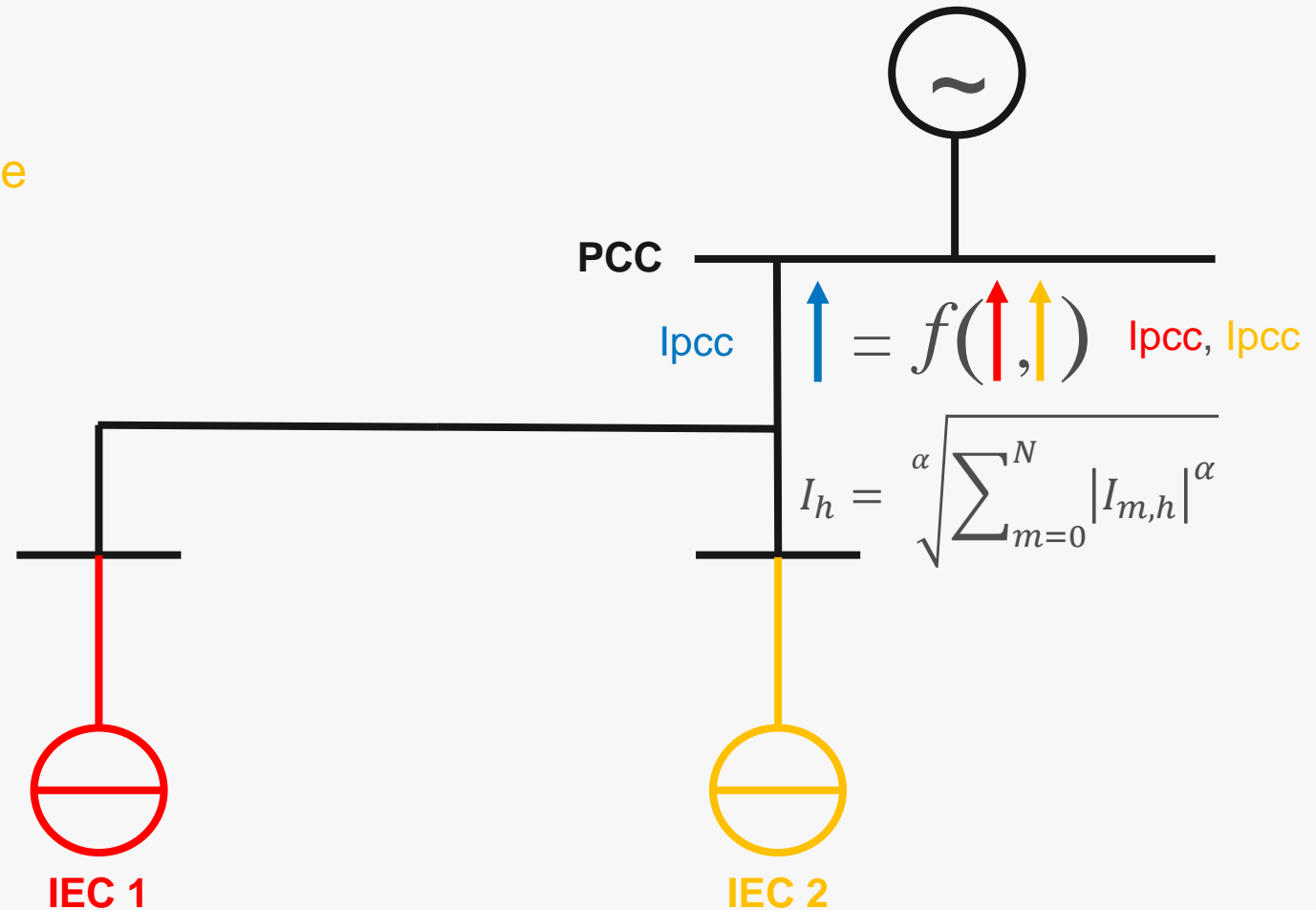

# Mix of phase correct and IEC sources

# Phase correct and IEC sources



1<sup>st</sup> calculation with only, but ALL phase correct sources (Complex Summation )

2<sup>nd</sup> calculation with only the first IEC source

3<sup>rd</sup> calculation with only the second IEC source

→ Sum up ALL individual harmonic currents and voltages of each calculation at all buses according to summation law

