


# Behaviour of a balanced load with YN-E

connection during presence of a negative sequence voltage

Assumption:

100% positive sequence voltage


100% negative sequence voltage

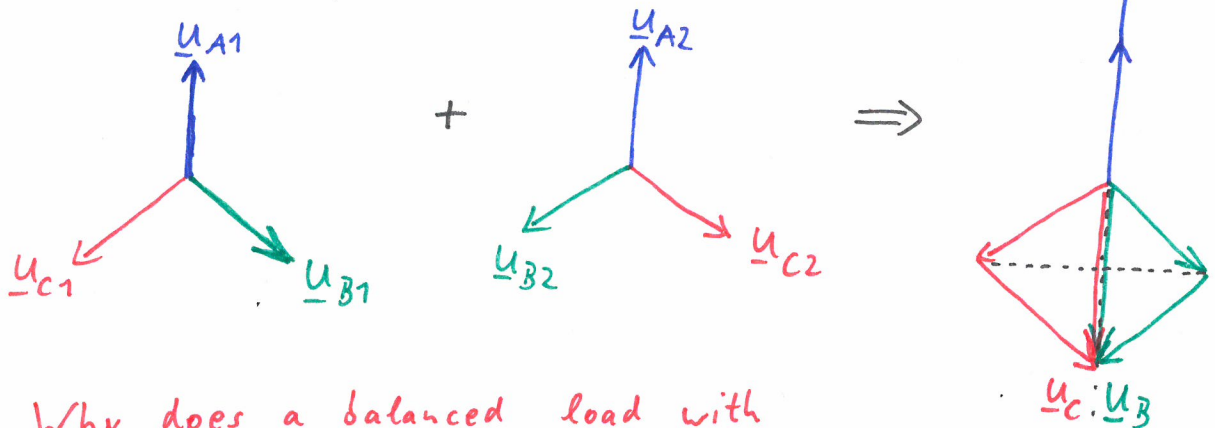

Why does a balanced load with constant power generate a zero sequence current flow if this voltage is applied?

$$\begin{aligned} \underline{U}_A &= 2 \cdot \underline{U}_{A1} \\ \underline{U}_B &= -\underline{U}_{A1} \\ \underline{U}_C &= -\underline{U}_{A1} \end{aligned}$$

Load with constant impedance

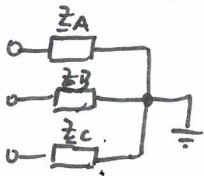

Assumption:  $Z_A = Z_B = Z_C = R$

$$\begin{aligned} \underline{I}_A &= \frac{\underline{U}_A}{Z_A} = \frac{2 \cdot \underline{U}_{A1}}{R} = 2 \cdot \underline{I}_{A1} \\ \underline{I}_B &= \frac{\underline{U}_B}{Z_B} = \frac{-\underline{U}_{A1}}{R} = -\underline{I}_{A1} \\ \underline{I}_C &= \frac{\underline{U}_C}{Z_C} = \frac{-\underline{U}_{A1}}{R} = -\underline{I}_{A1} \end{aligned}$$

$$\Rightarrow 3 \cdot \underline{I}_0 = \underline{I}_A + \underline{I}_B + \underline{I}_C = (2 - 1 - 1) \underline{I}_{A1} = 0$$

Load with constant power

Assumption:  $S_A = P_A$   
 $S_B = P_B = P_A$   
 $S_C = P_C = P_A$

$$\begin{aligned} \underline{I}_A &= \left( \frac{S_A}{\underline{U}_A} \right)^* = \left( \frac{P_A}{2 \cdot \underline{U}_{A1}} \right)^* = \frac{1}{2} \cdot \underline{I}_{A1} \\ \underline{I}_B &= \left( \frac{S_B}{\underline{U}_B} \right)^* = \left( \frac{P_A}{-\underline{U}_{A1}} \right)^* = -\underline{I}_{A1} \\ \underline{I}_C &= \left( \frac{S_C}{\underline{U}_C} \right)^* = \left( \frac{P_A}{-\underline{U}_{A1}} \right)^* = -\underline{I}_{A1} \end{aligned}$$

$$\Rightarrow 3 \cdot \underline{I}_0 = \underline{I}_A + \underline{I}_B + \underline{I}_C = \left( \frac{1}{2} - 1 - 1 \right) \underline{I}_{A1} = -1,5 \underline{I}_{A1}$$